

Code : 100302

**B.Tech 3rd Semester Exam., 2020  
(New Course)**

**ANALOG ELECTRONIC CIRCUITS**

Time : 3 hours

Full Marks : 70

Instructions :

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.
- (v) Symbols and notations carry their usual meanings.

1. Answer any seven questions of the following :

2×7=14

- (a) What is the function of clamping circuits?
- (b) Explain diode positive shunt clipper circuit with waveforms.
- (c) Write the important characteristics of common source configuration of JFET.

AK-21/190

( Turn Over )

( 2 )

- (d) Explain the half-wave rectifier with suitable diagram.
- (e) What is integrator circuit?
- (f) Write down the three differences between BJT and JFET.
- (g) Explain the important characteristics of Darlington emitter-follower.
- (h) What is precision rectifier circuit?
- (i) What are the advantages of h-parameters?

Answer any four questions. Attempt any two parts from each :

- 2. (a) Derive the expression for stability factor for fix bias circuit with respect to  $I_{CO}$ ,  $V_{BE}$  and  $\beta$ .
- (b) State and prove Miller's theorem.
- (c) A voltage divider biased circuit has  $R_1 = 39\text{ k}\Omega$ ,  $R_2 = 82\text{ k}\Omega$ ,  $R_C = 3.3\text{ k}\Omega$ ,  $R_E = 1\text{ k}\Omega$  and  $CC = 18\text{ V}$ . The silicon transistor has used  $\beta = 120$ . Find Q-point and stability factor. 7×2=14

AK-21/190

( Continued )

3. (a) An op-amp has gain bandwidth product of 15 MHz. Determine the bandwidth of op-amp when  $A_{CL} = 500$ . Also, find the maximum value of  $A_{CL}$  when frequency is 200 KHz. <https://www.akubihar.com>

- (b) What are the advantages and features of instrumentation amplifier? Derive the expression for output voltage of instrumentation amplifier.

- (c) The data sheet of  $N$ -channel JFET gives the following details :

$I_{DSS} = 9\text{mA}$  and pinch-off voltage  $= -4.5\text{V}$

- (i) At what value of  $V_{GS}$  will  $I_D$  be equal to 3 mA?

- (ii) What is its  $g_m$  at this  $I_D$ ?  $7 \times 2 = 14$

4. (a) Derive an expression for input impedance voltage gain, current gain and output impedance for an emitter-follower circuit using  $h$ -parameter model for the transistor.

- (b) Explain the need of cascading amplifier. Draw and explain the block diagram of two-stage cascade amplifier.

- (c) Derive an expression for frequency of oscillators in Wien bridge oscillator.

$7 \times 2 = 14$

5. (a) Explain the principle of operation of oscillator and effect of loop gain ( $A\beta$ ) on the output of oscillator.

- (b) With the help of neat diagram, explain the construction working and characteristics of  $N$ -channel depletion-type MOSFET.

- (c) A given amplifier arrangement has the following voltage gains :

$$A_{v1} = 10, A_{v2} = 20 \text{ and } A_{v3} = 40$$

Calculate the overall voltage gain and determine the total voltage gain in dB.

$7 \times 2 = 14$

6. (a) Determine  $Z_{in}$ ,  $Z_{out}$  and  $A_v$  for JFET common source amplifier with fixed bias configuration using AC equivalent small signal model.
- (b) With the help of neat diagram, explain the construction working and characteristics of  $N$ -channel JFET.
- (c) Explain the low frequency response of single-stage RC-coupled amplifier.  $7 \times 2 = 14$
7. (a) Obtain an  $h$ -parameter equivalent circuit of CB and CE configurations.
- (b) With the help of block diagram, explain the concept of feedback.
- (c) Discuss with the help of circuit example, the purpose of providing—  
 (i) negative feedback;  
 (ii) positive feedback in amplifier.  $7 \times 2 = 14$
8. (a) Draw the high frequency equivalent circuit of an emitter follower and derive the expression of upper cut-off frequency  $f_H$ .

- (b) Transistor's short circuit current gain is measured to be 25 at a frequency of 2 MHz. If  $f_B = 200$  kHz, calculate the following :
- (i) The current gain bandwidth product
- (ii)  $h_{fe}$  at low frequency
- (iii) Short circuit current gain at 10 MHz and 100 MHz
- (c) A phase-shift oscillator uses three identical  $R$ - $C$  sections in feedback network. The value of components are  $R = 100 \text{ k}\Omega$  and  $C = 0.01 \mu\text{F}$ . Calculate the frequency of oscillator.  $7 \times 2 = 14$
9. (a) An amplifier has a voltage gain of 40. The amplifier is now modified to provide a 10% negative feedback in series with the input. Determine the following :
- (i) Voltage gain with feedback
- (ii) Amount of feedback in dB
- (iii) Loop gain

( 7 )

- (b) Write the important advantage of a negative feedback amplifier and show that how bandwidth of an amplifier increases with negative feedback.
- (c) What is transistor biasing? Explain emitter bias circuit with relevant circuit and equations.  $7 \times 2 = 14$

★ ★ ★

<https://www.akubihar.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजें और 10 रुपये पायें,

Paytm or Google Pay से